

# Assignment - 2

Name : Aparajita Biswas

ID : 2023200000174

Problem : 1 - Design an amplifier using your assigned BJT.

Solve :

Here, The last 3 digit of my ID is : 174

Sum of the 3 digit is :  $(1 + 7 + 4) = 12$  (even)


So, the BJT is BC547C

From datasheet,  $I_c = 2 \text{ mA}$ ,  $V_{CE} = 5.0 \text{ V}$

$$\therefore V_{cc} = 2V_{CE} = (2 \times 5) = 10 \text{ V}$$

$$\beta = 420$$

Circuit :

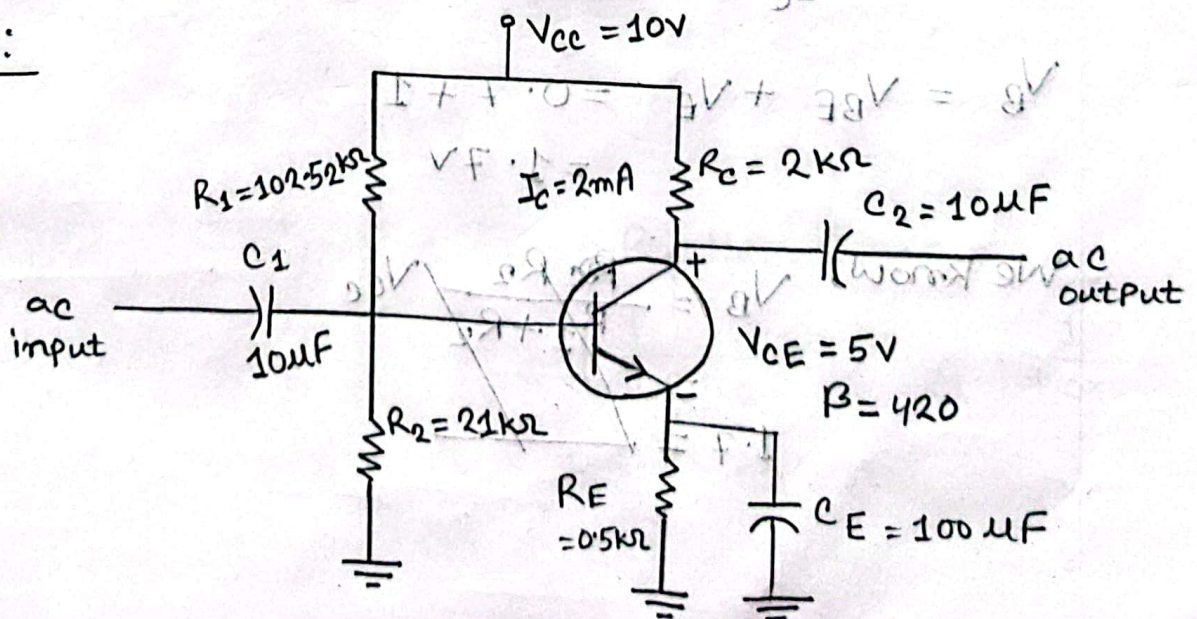



## 2-transistor

We know,  $V_E = \frac{1}{10} V_{CC} = \frac{1}{10} \times 10 = 1V$

Now,  $I_E = \frac{V_E}{R_E}$

$\therefore R_E = \frac{V_E}{I_E}$

$\Rightarrow R_E = \frac{V_E}{I_C} \quad [\because I_E \cong I_C]$

$= \frac{1}{2 \times 10^{-3}}$

$= 500 \Omega = 0.5 k\Omega$

$I_B = \frac{I_C}{\beta} = \frac{2}{420} = 4.76 \times 10^{-3} mA$

$V_{RE} = V_{CC} - V_{CE} - V_E = (10 - 5 - 1) = 4V$

$\therefore R_C = \frac{V_{RE}}{I_C} = \frac{4}{2 \times 10^{-3}} = 2000 \Omega = 2k\Omega$

$V_B = V_{BE} + V_E = 0.7 + 1 = 1.7V$

Now,  $\beta R_E \geq 10 R_2$

$$\Rightarrow R_2 \leq \frac{1}{10} \beta R_E$$

$$\Rightarrow R_2 \leq \frac{1}{10} \times 420 \times 0.5$$

$$\Rightarrow R_2 \leq 21 \text{ k}\Omega \quad \therefore R_2 = 21 \text{ k}\Omega$$

We know,  $V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$

$$\Rightarrow 1.7 = \frac{21 \times 15}{R_1 + 21}$$

$$\therefore R_1 = 102.52 \text{ k}\Omega$$

Here,  $r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2 \text{ mA}} = 13 \Omega$

$$= \frac{26 \text{ mV}}{I_C} \quad [\because I_C \cong I_E]$$

$$= \frac{26 \text{ mV}}{2.0 \text{ mA}}$$

$$= 13 \Omega$$

$$= 0.013 \text{ k}\Omega$$

Here, input impedance,  $Z_{in} = R_1 \parallel R_2 \parallel \beta r_e$

$$= \left( \frac{1}{102.52} + \frac{1}{21} + \frac{1}{420 \times 0.013} \right)^{-1}$$

$$= 4.1575 \text{ k}\Omega$$



Output impedance,  $Z_{out} = R_c \parallel r_o$

$$= \left( \frac{1}{R_c} + \frac{1}{r_o} \right)^{-1}$$

$$= \left( \frac{1}{R_c} + \frac{1}{\infty} \right)^{-1} [r_o \approx \infty]$$

$$= \left( \frac{1}{R_c} \right)^{-1} = \left( \frac{1}{2} \right)^{-1}$$

$$= 2 \text{ k}\Omega$$

Input AC  $V = (1+7+4) \div 3 = 4 \text{ mV}$

Here,  $A_v = \frac{V_o}{V_s} = \frac{486.27}{4}$  [Peak value : 486.27 mV]  
 $= 121.56$

Problem 2: Design a relay module

Solve:

ID is : 174

sum is :  $(1+7+4) = 12$  (even)




So, I have to design 9V relay module.

From datasheet of SRD-09VDC-SL-C relay,

$$I_{c,sat} = 50 \text{ mA}$$

For BC547C BJT,  $\beta = 430$  (400 to 600)

Here,  $V_i = 5 \text{ V}$

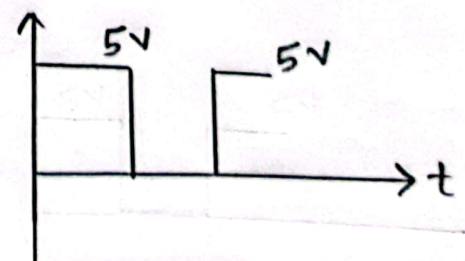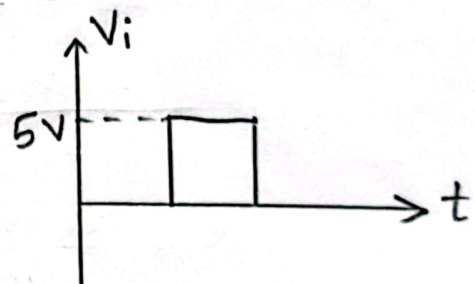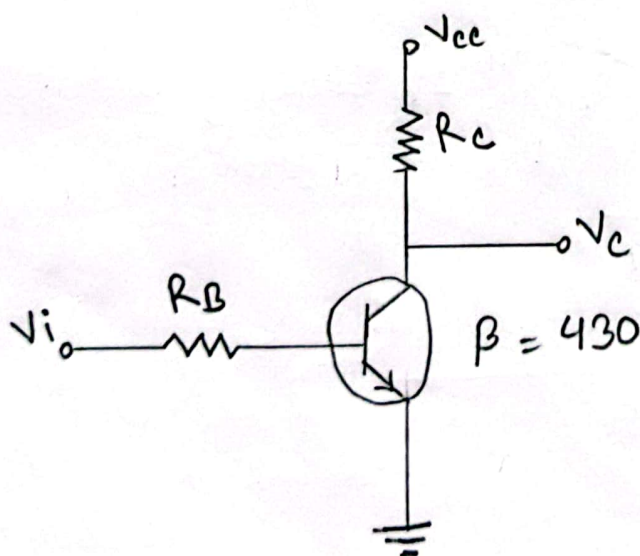



$$I_B' = \frac{I_{csat}}{\beta} = \frac{50 \times 10^{-3}}{430}$$

$$= 116.27 \mu A$$

$$I_B > I_B'$$

$$\text{So, } I_B = 232.54 \mu A$$

$$\therefore R_B = \frac{V_i - 0.7}{I_B} = \frac{5 - 0.7}{232.54 \times 10^{-6}} = 18.491 \text{ k}\Omega$$

